



Università degli Studi di Napoli Federico II  
Scuola Politecnica e delle Scienze di Base

# Esame ASDI

SIMONE D'ORTA

# Sommario

1 Traccia .....	2
2 Soluzione .....	2
3 Codice.....	4
3.1 Unità A .....	4
3.1.1 Unità operativa .....	6
3.1.2 Unità di controllo .....	8
3.2 Unità B.....	10
3.2.1 Unità operativa .....	12
3.2.2 Unità di controllo .....	14
3.3 Top Module.....	16
4 Simulazione .....	17

# 1 Traccia


Un'unità A invia a un'unità B N coppie di byte da addizionare, prelevando il primo byte  $X_i$  di ciascuna coppia da una memoria ROM1 e l'altro  $Y_i$  da una seconda memoria ROM2. I byte vengono trasmessi a B mediante un protocollo di handshaking effettuato bit a bit, inviando prima un bit di  $X_i$  e poi uno di  $Y_i$ . Per ogni coppia di bit ricevuti, l'unità B li passa ad un sommatore seriale.

Si progetti ed implementi in VHDL il sistema complessivo, avendo cura di includere due componenti contatore in A (uno che conta le coppie inviate e l'altro utilizzato per la trasmissione bit a bit) e un componente contatore e uno sommatore in B.

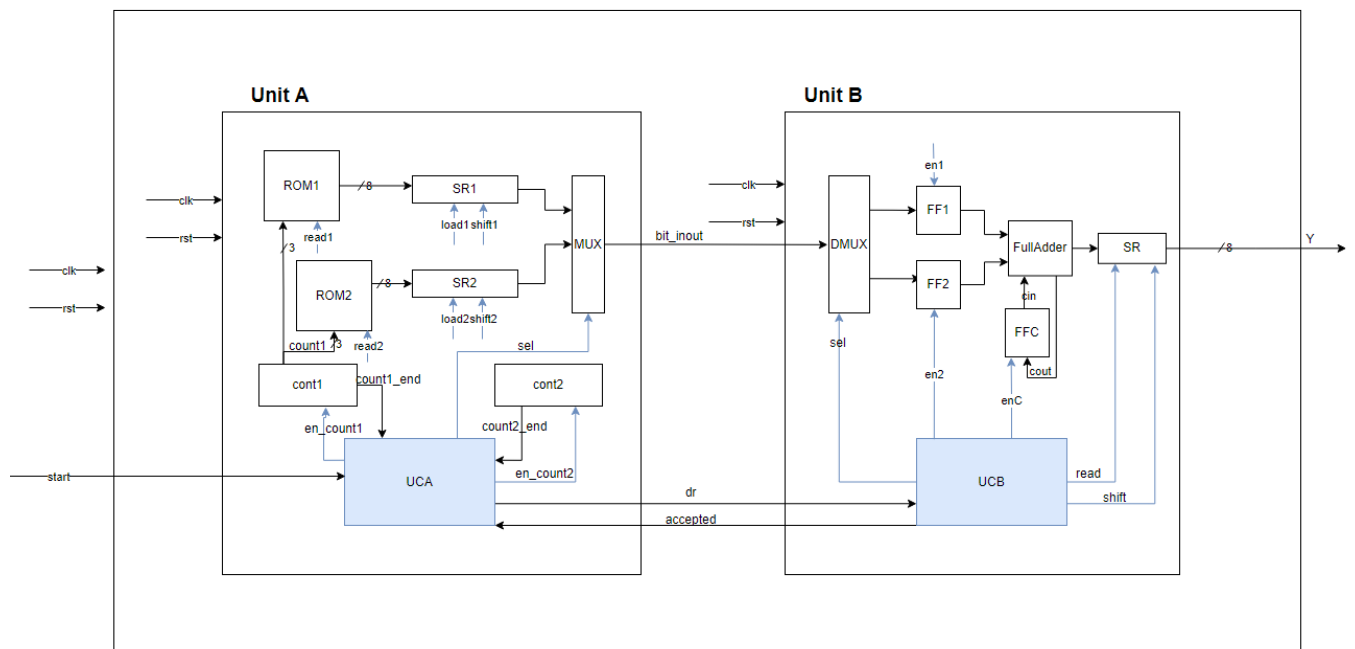
# 2 Soluzione

Ogni singola unità è stata decomposta in unità operativa e unità di controllo.


Le due unità sono state poi collegate all'interno di un top module.



 
Le due unità di controllo, oltre a gestire le unità operative, implementano un protocollo di handshake tramite i segnali *dr* (data ready) e *accepted*.



## AUTOMA CONTROLLER A

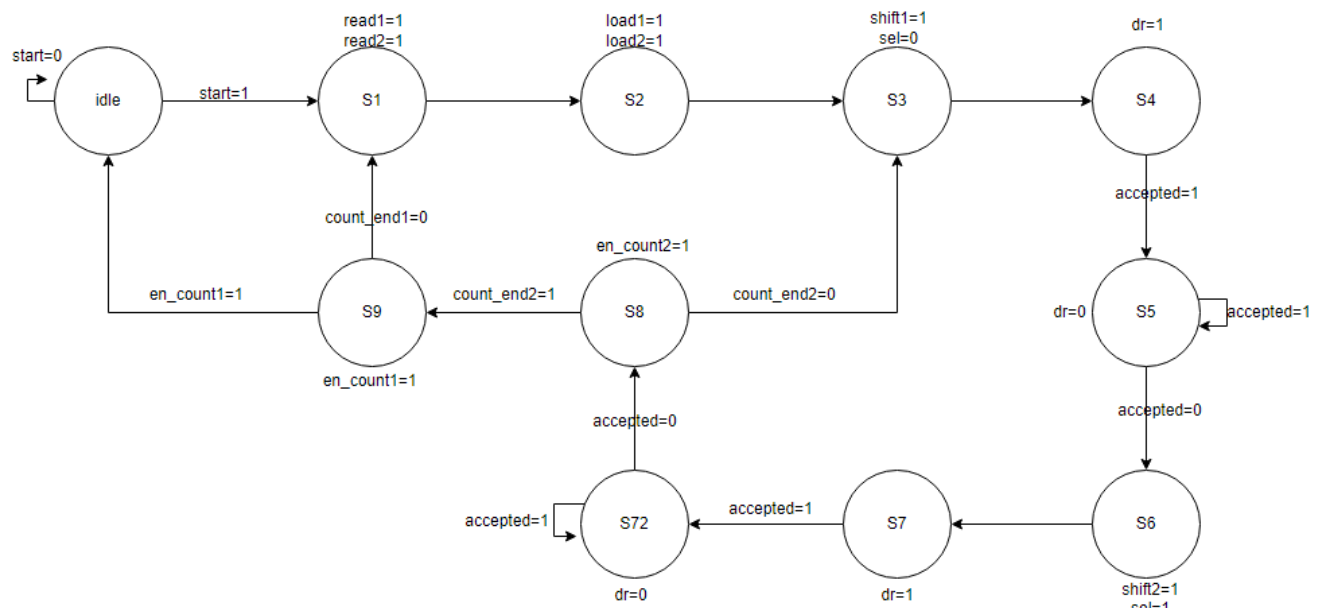

## AUTOMA CONTROLLER B

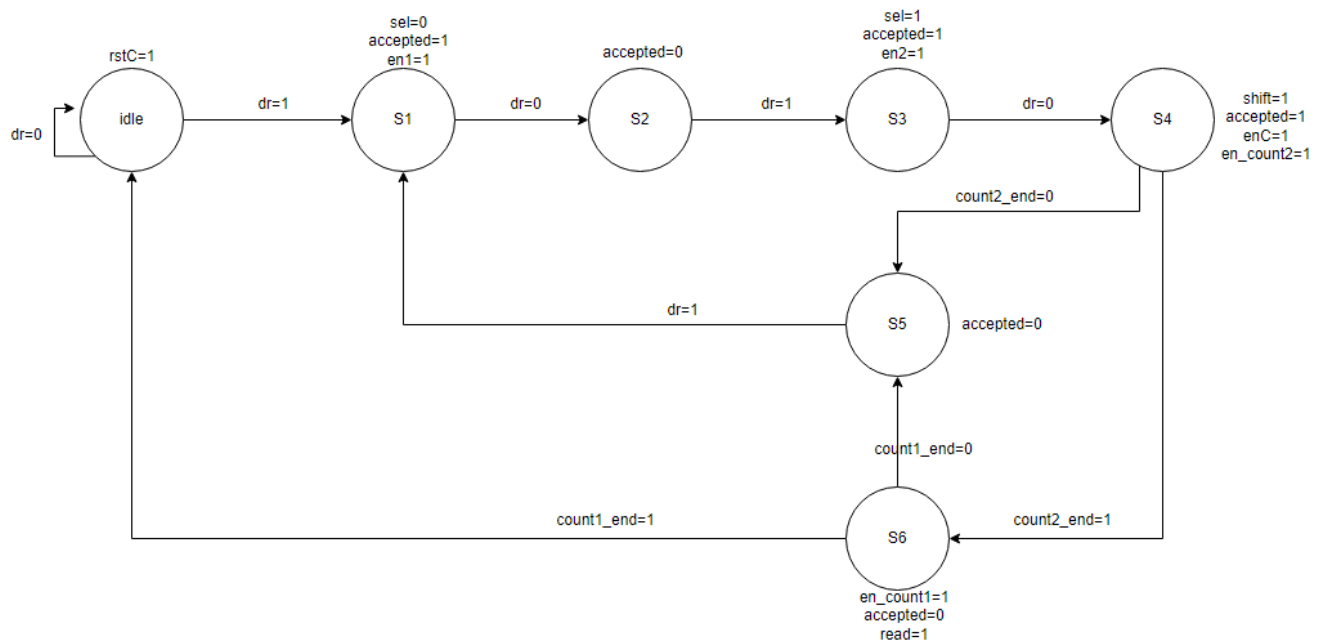

## 3 Codice

### 3.1 Unità A

```
entity unitA is
    Port (
        clk, rst, start: in std_logic;
        accepted: in std_logic;
        dr, bit_out: out std_logic
    );
end unitA;

architecture structural of unitA is

    component Cont8 is
        Port (
            clock, reset: in std_logic;
            count_in: in std_logic;
            count_end: out std_logic;
            count: out std_logic_vector(2 downto 0)
        );
    end component;

    component ROM is
    port(
        CLK : in std_logic; -- clock della board
        RST : in std_logic;
        READ : in std_logic; -- segnale che abilita la lettura
        ADDR : in std_logic_vector(2 downto 0); --3 bit di indirizzamento
        DATA : out std_logic_vector(7 downto 0) -- dato su 8 bit
    );
    end component;

    component ROM2 is
    port(
        CLK : in std_logic; -- clock della board
        RST : in std_logic;
        READ : in std_logic; -- segnale che abilita la lettura
        ADDR : in std_logic_vector(2 downto 0); --3 bit di indirizzamento
        DATA : out std_logic_vector(7 downto 0) -- dato su 8 bit
    );
    end component;
```

```

component parallel_in_serial_out is
    port(
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        load, shift : in STD_LOGIC;
        din : in STD_LOGIC_VECTOR(7 downto 0);
        dout : out STD_LOGIC
    );
end component;

component mux2_1 is
    Port ( x0 : in STD_LOGIC;
           x1 : in STD_LOGIC;
           sel : in STD_LOGIC;
           y0 : out STD_LOGIC);
end component;

component control_unitA is
    Port (
        clk, rst, start: in std_logic;
        count_end1, count_end2: in std_logic;
        accepted: in std_logic;
        read1, read2, load1, load2, shift1, shift2: out std_logic;
        en_count1, en_count2: out std_logic;
        sel, dr: out std_logic
    );
end component;

signal srl_out, sr2_out, sel: std_logic;
signal rom1_out, rom2_out: std_logic_vector(7 downto 0);
signal count1, count2: std_logic_vector(2 downto 0);
signal en_count1, en_count2, read1, read2: std_logic;
signal load1, load2, shift1, shift2: std_logic;
signal count_end1, count_end2: std_logic;

begin
mux: mux2_1 port map(srl_out, sr2_out, sel, bit_out);
r1: ROM port map(clk, rst, read1, count1, rom1_out);
r2: ROM2 port map(clk, rst, read2, count1, rom2_out);
srl: parallel_in_serial_out port map(clk, rst, load1, shift1, rom1_out, srl_out);
sr2: parallel_in_serial_out port map(clk, rst, load2, shift2, rom2_out, sr2_out);
c1: cont8 port map(clk, rst, en_count1, count_end1, count1);
c2: cont8 port map(clk, rst, en_count2, count_end2, count2);
cu: control_unitA port map(clk, rst, start, count_end1, count_end2, accepted, read1, read2, load1, load2,
                           shift1, shift2, en_count1, en_count2, sel, dr);

```

### 3.1.1 Unità operativa

Mux:

```
entity mux2_1 is
    Port ( x0 : in STD_LOGIC;
          x1 : in STD_LOGIC;
          sel : in STD_LOGIC;
          y0 : out STD_LOGIC);
end mux2_1;

architecture rtl of mux2_1 is

begin
    y0 <= x0 when sel = '0' else
        x1 when sel = '1' else
            '-';

end rtl;
```

ROM:

```
entity ROM is
port(
    CLK : in std_logic; -- clock della board
    RST : in std_logic;
    READ : in std_logic; -- segnale che abilita la lettura, inserito
    ADDR : in std_logic_vector(2 downto 0); -- 3 bit di indirizzo per
    DATA : out std_logic_vector(7 downto 0) -- dato su 8 bit letto da
);
end ROM;
-- creo una ROM di 8 elementi da 8 bit ciascuno
architecture behavioral of ROM is
type rom_type is array (7 downto 0) of std_logic_vector(7 downto 0);
signal ROM : rom_type := (
    X"4A",
    X"49",
    X"01",
    X"DD",
    X"34",
    X"02",
    X"1E",
    X"26");

attribute rom_style : string;
attribute rom_style of ROM : signal is "block";-- block dice al tool
-- distributed di usare
begin

process(CLK)
begin
    if rising_edge(CLK) then
        if (RST = '1') then
            DATA <= ROM(conv_integer("000"));
        elsif (READ = '1') then
            DATA <= ROM(conv_integer(ADDR));
        end if;
    end if;
end process;
end behavioral;
```

### Shift register PISO:

```
entity parallel_in_serial_out is
    port(
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        load, shift : in STD_LOGIC;
        din : in STD_LOGIC_VECTOR(7 downto 0);
        dout : out STD_LOGIC
    );
end parallel_in_serial_out;

architecture piso_arc of parallel_in_serial_out is

    signal temp: std_logic_vector(7 downto 0);

begin

    piso : process (clk,reset) is
    begin
        if (reset='1') then
            temp <= (others=>'0');
        elsif (clk'event and clk='1') then
            if (load='1') then
                temp <= din ;
            elsif (shift='1') then
                dout <= temp(0);
                temp <= '0'&temp(7 downto 1);
            end if;
        end if;
    end process piso;

end piso_arc;
```

### Contatore modulo 8:

```
entity Cont8 is
    Port (
        clock, reset: in std_logic;
        count_in: in std_logic;
        count_end: out std_logic;
        count: out std_logic_vector(2 downto 0)
    );
end Cont8;

architecture Behavioral of Cont8 is

    signal c: std_logic_vector(2 downto 0):="000";

begin

    CM8: process(clock)
    begin
        if(clock'event and clock='1') then
            if(reset='1') then
                c<=(others=>'0');
                count_end<='0';
            elsif(count_in='1') then
                c<=std_logic_vector(unsigned(c)+1);
                if(c="111") then count_end<='1';
                else count_end<='0';
                end if;
            end if;
        end if;
    end process;

    count <= c;

end Behavioral;
```



### 3.1.2 Unità di controllo

```
entity control_unitA is
    Port (
        clk, rst, start: in std_logic;
        count_end1, count_end2: in std_logic;
        accepted: in std_logic;
        read1, read2, load1, load2, shift1, shift2: out std_logic;
        en_count1, en_count2: out std_logic;
        sel, dr: out std_logic
    );
end control_unitA;

architecture automa of control_unitA is

    type state is (idle, S1, S2, S3, S4, S5, S6, S7, S72, S8, S9);
    signal current_state: state := idle;
    signal next_state: state;

begin

    reg: process (clk)
    begin
        if (clk'event and clk='0') then
            if (rst='1') then
                current_state<=idle;
            else
                current_state<=next_state;
            end if;
        end if;
    end process;

    comb: process (start, accepted, count_end1, count_end2, current_state)
    begin
        en_count1<='0';
        en_count2<='0';
        read1<='0';
        read2<='0';
        load1<='0';
        load2<='0';
        shift1<='0';
        shift2<='0';
        dr<='0';
        case current_state is
            when idle =>
                if (start='1') then
```

```

        next_state<=S1;
    else    next_state<=idle;
    end if;
when S1 =>  read1<='1';
            read2<='1';
            next_state<=S2;
when S2 =>  load1<='1';
            load2<='1';
            next_state<=S3;
when S3 =>  shift1<='1';
            sel<='0';
            next_state<=S4;
when S4 =>  dr<='1';
            if(accepted='1') then
                next_state<=S5;
            end if;
when S5 =>  dr<='0';
            if(accepted='0') then
                next_state<=S6;
            end if;
when S6 =>  shift2<='1';
            sel<='1';
            next_state<=S7;
when S7 =>  dr<='1';
            if(accepted='1') then
                next_state<=S72;
            end if;
when S72 => dr<='0';
            if(accepted='0') then
                next_state<=S8;
            end if;
when S8 =>  en_count2<='1';
            if(count_end2='1') then
                next_state<=S9;
            elsif (count_end2='0') then
                next_state<=S3;
            end if;
when S9 =>  en_count1<='1';
            if(count_end1='1') then
                next_state<=idle;
            elsif (count_end1='0') then
                next_state<=S1;
            end if;
end case;

```

### 3.2 Unità B

```
entity unitB is
  Port (
    clk, rst: in std_logic;
    dr, bit_in: in std_logic;
    accepted: out std_logic;
    Y: out std_logic_vector(7 downto 0)
  );
end unitB;

architecture structural of unitB is

  component serial_in_parallel_out is
    port(
      clk : in STD_LOGIC;
      reset : in STD_LOGIC;
      read, shift : in STD_LOGIC;
      din : in STD_LOGIC;
      dout : out STD_LOGIC_VECTOR(7 downto 0)
    );
  end component;

  component full_adder is
    port(
      a,b: in std_logic;
      cin: in std_logic;
      cout, s: out std_logic);
  end component;

  component demux_12 is
    port ( X: in std_logic;
      s: in std_logic; --ingresso di selezione
      Y0, Y1: out std_logic
    );
  end component;

  component FFD is
    port(
      Q : out std_logic;
      clk, rst :in std_logic;
      D, en :in std_logic
    );
  end component;
```

```

component Cont8 is
  Port (
    clock, reset: in std_logic;
    count_in: in std_logic;
    count_end: out std_logic;
    count: out std_logic_vector(2 downto 0)
  );
end component;

component control_unitB is
  Port (
    clk, rst: in std_logic;
    dr, count1_end, count2_end: in std_logic;
    rstC, accepted, en1, en2, enC: out std_logic;
    shift, read, en_count1, en_count2, sel: out std_logic
  );
end component;

signal sel, en1, en2, enC, a, b, rstC: std_logic;
signal y1, y2, cin, cout, s, count1_end, count2_end: std_logic;
signal count1, count2: std_logic_vector(2 downto 0);
signal en_count1, en_count2, shift, read: std_logic;

begin
ff1: FFD port map(a, clk, rst, y1, en1);
ff2: FFD port map(b, clk, rst, y2, en2);
ffC: FFD port map(cin, clk, rstC, cout, enC);
demux: demux_12 port map(bit_in, sel, y1, y2);
fa: full_adder port map(a, b, cin, cout, s);
c1: cont8 port map(clk, rst, en_count1, count1_end, count1);
c2: cont8 port map(clk, rst, en_count2, count2_end, count2);
sr: serial_in_parallel_out port map(clk, rst, read, shift, s, Y);
cu: control_unitB port map(clk, rst, dr, count1_end, count2_end, rstC, accepted, en1,
                          en2, enC, shift, read, en_count1, en_count2, sel);

end structural;

```

### 3.2.1 Unità operativa

Flip Flop D:

```
entity FFD is
  port(
    Q : out std_logic;
    clk, rst :in std_logic;
    D, en :in std_logic
  );
end FFD;
architecture Behavioral of FFD is
begin
  process(clk)
  begin
    if(rising_edge(clk)) then
      if(rst='1') then
        Q <= '0';
      elsif(en='1') then
        Q <= D;
      end if;
    end if;
  end process;
end Behavioral;
```

Demultiplexer:

```
entity demux_12 is
port ( X: in std_logic;
       s: in std_logic; --ingresso di selezione
       Y0, Y1: out std_logic
    );
end demux_12;

architecture Behavioral of demux_12 is

begin

process(X,s)
begin
if (s = '0') then
  Y0 <= X;
  Y1 <= '0';
elsif (s = '1') then
  Y0 <= '0';
  Y1 <= X;
end if;
end process;
end Behavioral;
```

Full adder:

```
entity full_adder is
    port(
        a,b: in std_logic;
        cin: in std_logic;
        cout, s: out std_logic);
end full_adder;

architecture rtl of full_adder is

    begin

        s<= a xor b xor cin;
        cout<= (a and b) or (cin and (a xor b));

    end rtl;
```

Shift register SIPO:

```
entity serial_in_parallel_out is
    port(
        clk : in STD_LOGIC;
        reset : in STD_LOGIC;
        read, shift : in STD_LOGIC;
        din : in STD_LOGIC;
        dout : out STD_LOGIC_VECTOR(7 downto 0)
    );
end serial_in_parallel_out;

architecture behavioral of serial_in_parallel_out is

    signal temp: std_logic_vector(7 downto 0):=X"00";

begin

    process (clk,reset) is
    begin
        if (reset='1') then
            temp <= (others=>'0');
            dout <= (others=>'0');
        elsif (clk'event and clk='1') then
            if (read='1') then
                dout <= temp ;
            elsif (shift='1') then
                temp <= din&temp(7 downto 1);
            end if;
        end if;
    end process piso;

end behavioral;
```

### 3.2.2 Unità di controllo

```
entity control_unitB is
  Port (
    clk, rst: in std_logic;
    dr, count1_end, count2_end: in std_logic;
    rstC, accepted, en1, en2, enC: out std_logic;
    shift, read, en_count1, en_count2, sel: out std_logic
  );
end control_unitB;

architecture automa of control_unitB is
|
  type state is (idle, S1, S2, S3, S4, S5, S6);
  signal current_state: state := idle;
  signal next_state: state;

begin

  reg: process (clk)
  begin
    if (clk'event and clk='0') then
      if (rst='1') then
        current_state<=idle;
      else
        current_state<=next_state;
      end if;
    end if;
  end process;

  comb: process (dr, count1_end, count2_end, current_state)
  begin
    en_count1<='0';
    en_count2<='0';
    shift<='0';
    accepted<='0';
    en1<='0';
    en2<='0';
    enC<='0';
    rstC<='0';
    sel<='0';
    read<='0';
    case current_state is
      when idle => rstC<='1';
        if (dr='1') then
          next_state<=S1;
        end if;
    end case;
  end process;
end automa;
```

```

        else
            next_state<=idle;
        end if;
when S1 => en1<='1';
            accepted<='1';
            sel<='0';
            if(dr='0') then
                next_state<=S2;
            end if;
when S2 => accepted<='0';
            if(dr='1') then
                next_state<=S3;
            end if;
when S3 => sel<='1';
            accepted<='1';
            en2<='1';
            if(dr='0') then
                next_state<=S4;
            end if;
when S4 => shift<='1';
            enC<='1';
            en_count2<='1';
            accepted<='1';
            if(count2_end='1') then
                next_state<=S6;
            elsif(count2_end='0') then
                next_state<=S5;
            end if;
when S5 => if(dr='1') then
            next_state<=S1;
        end if;
when S6 => en_count1<='1';
            read<='1';
            if(count1_end='1') then
                next_state<=idle;
            elsif(count1_end='0') then
                next_state<=S5;
            end if;
        end case;
    end process;

end automa;

```



### 3.3 Top Module

```
entity TopModule is
  Port (
    clk, rst, start: in std_logic;
    Y: out std_logic_vector(7 downto 0)
  );
end TopModule;

architecture structural of TopModule is

  component unitA is
    Port (
      clk, rst, start: in std_logic;
      accepted: in std_logic;
      dr, bit_out: out std_logic
    );
  end component;

  component unitB is
    Port (
      clk, rst: in std_logic;
      dr, bit_in: in std_logic;
      accepted: out std_logic;
      Y: out std_logic_vector(7 downto 0)
    );
  end component;

  signal accepted, dr, bit_inout: std_logic;

begin
  A: unitA port map(clk, rst, start, accepted, dr, bit_inout);
  B: unitB port map(clk, rst, dr, bit_inout, accepted, Y);
end structural;
```

# 4 Simulazione

ROM1 = 26, 1E, 02, 34, DD, 01, 49, 41


ROM2 = 73, 24, 23, 01, 11, F3, 20, 01

Y = 99, 42, 25, 35, EE, F4, 72, 4B

```
stimulus: process
begin

    wait for 20ns;
    rst<='0';
    start<='1';
    wait for 50ns;
    start<='0';
    wait for 5400ns;
    rst<='1';
    wait for 20ns;
    rst<='0';
    wait for 10ns;
    start<='1';
    wait for 50ns;
    start<='0';

    wait;
end process;
```

 

Dettaglio della singola iterazione:

